PROJECT PROGRESS LOG

UGV-1

Team Members

G.N.S.S.Rithvik
R.Srikar Varshit

Roll Numbers

EE26BTECH11211
EE26BTECH11223

November 2, 2026

1 Assembling:

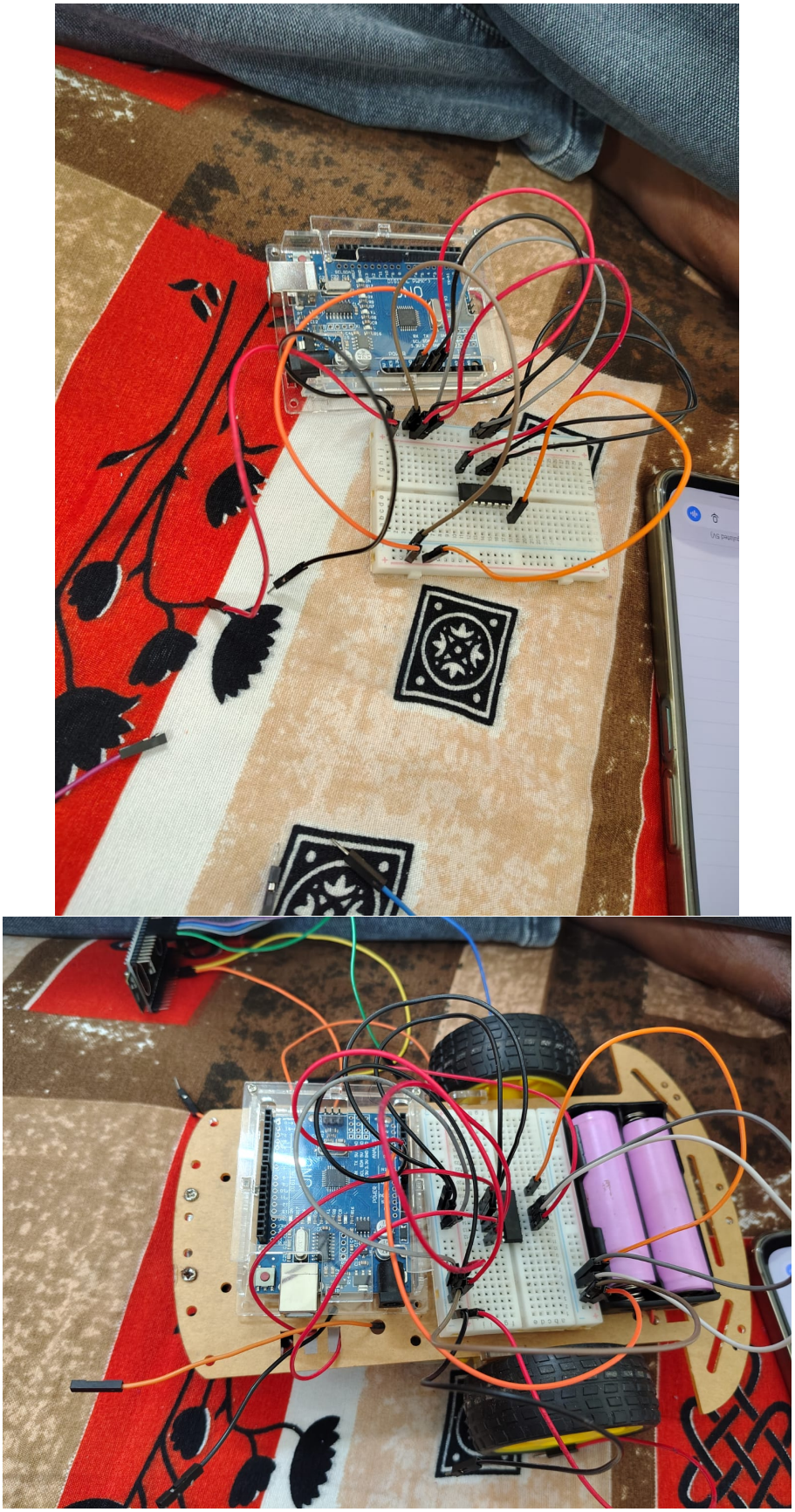


Figure 1: Initial connection

1.1 Workdone:

Initially we connected the arduino to the Motor Driver on the breadboard. Then we took some jumpers and we connected the ESP-32 to the Motor Driver and arduino and left it hanging in mid air.

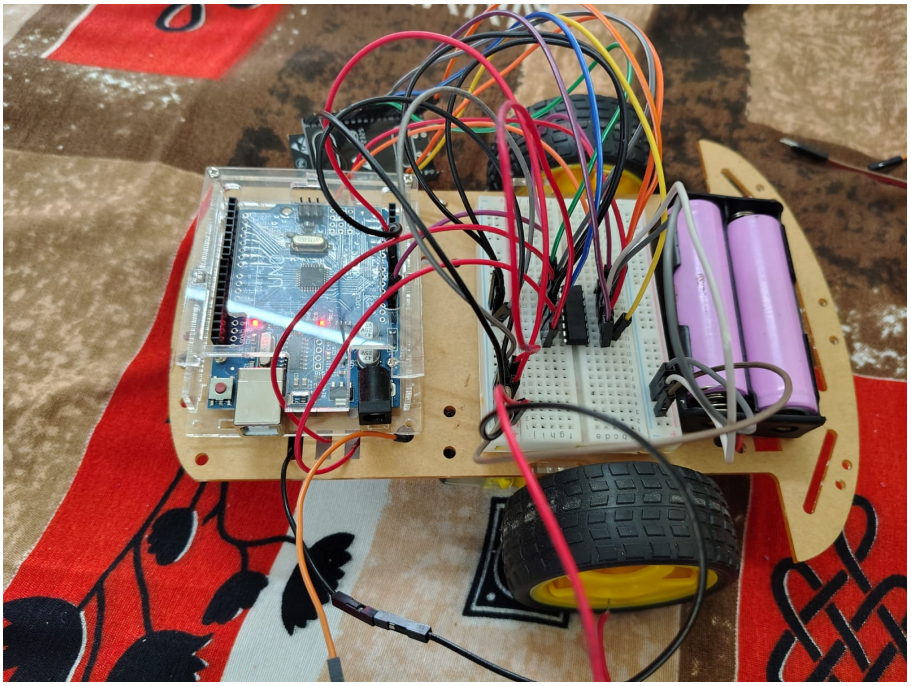


Figure 2: Initial problem faced

1.2 Observation:

After completing the connection we observed that the ESP-32 wouldn't glow. Then we thought there there might be a loose connection (or) there might be some non working jumber wires.

1.3 Workdone:

Then we removed the whole set up shown in figure 2.Then we thought of giving direct connection to ESP-32 from arduino and Motor Driver on the breadboard, not using jumper wires in between.

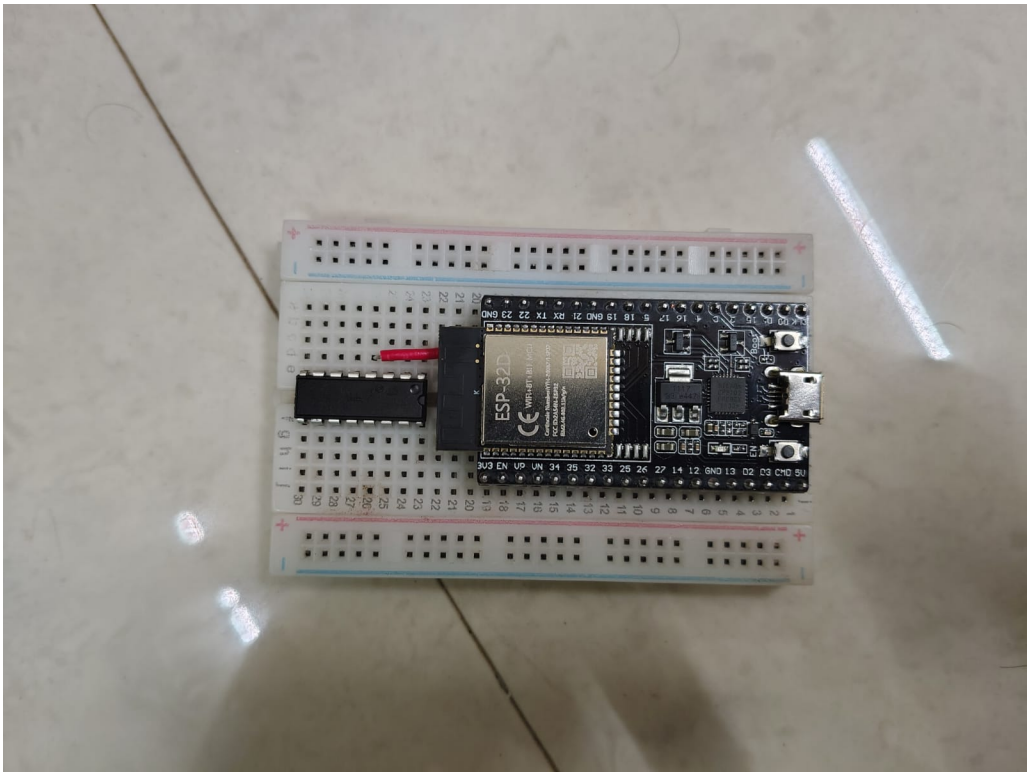


Figure 3: Assembling the ESP-32 and the motor driver on the breadboard

1.4 Workdone:

We assembled the ESP-32 and the motor driver on the breadboard as shown in Figure 3. The red wire in the figure 3 is the wire connecting to the GND of the ESP-32.

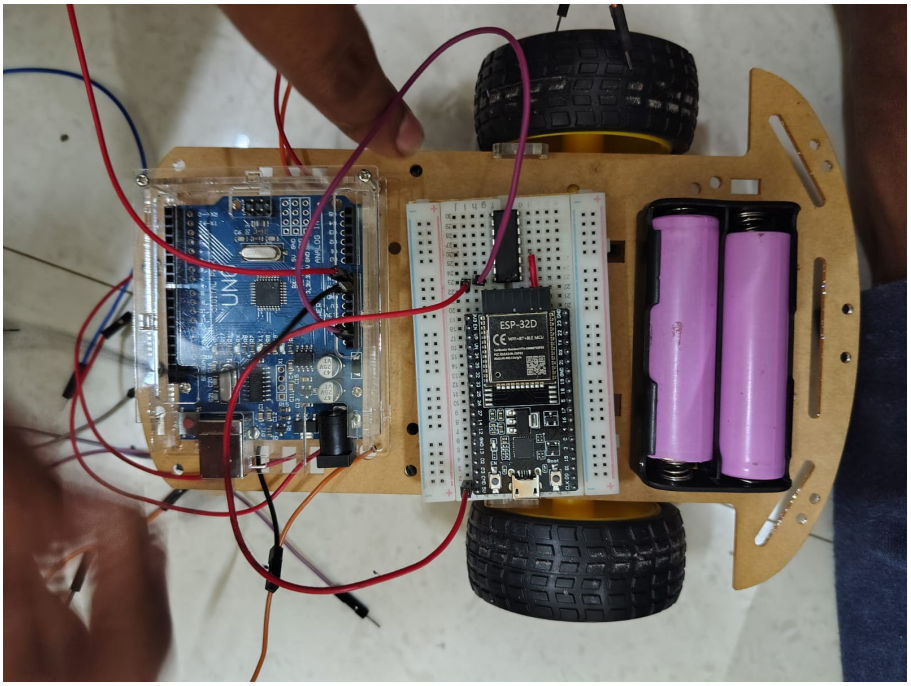


Figure 4: Using Arduino and connecting it to the breadboard

1.5 Workdone:

Then we connected the arduino to the breadboard. We are using the arduino as a voltage stabilizer. It receives the high voltage by the batteries as power input and gives as 5V output to the ESP-32 as power.

1.6 Workdone:

We powered the ESP-32 with arduino as shown in Figure 4.

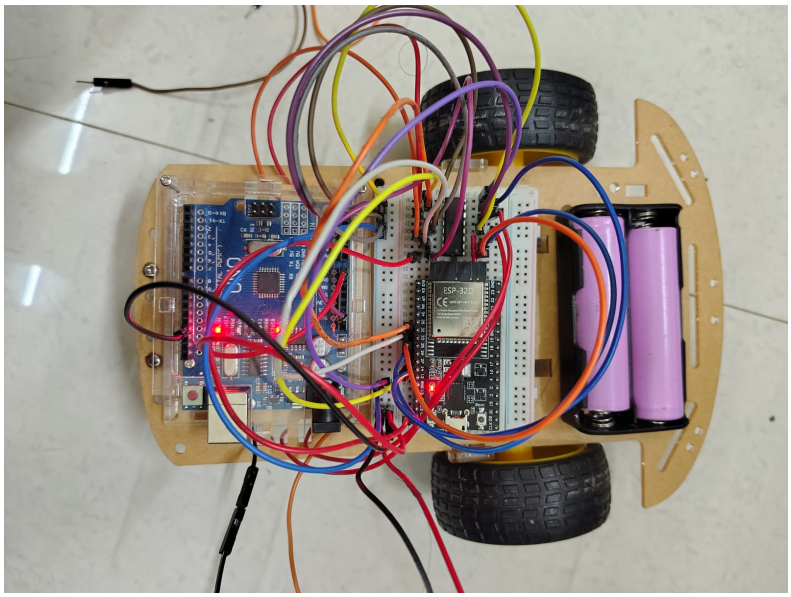


Figure 5: Complete connection of the circuit

1.7 Workdone:

After giving power from the arduino to ESP-32 and the Motor Driver.

1.8 Observation:

We observed that there is short circuit occuring when given power.It got short circuited when we gave direct connection between the batteries and ESP-32,Motor Driver. We observed that the led on the ESP-32 is glowing continously, Unlike when we gave it a direct connection.